
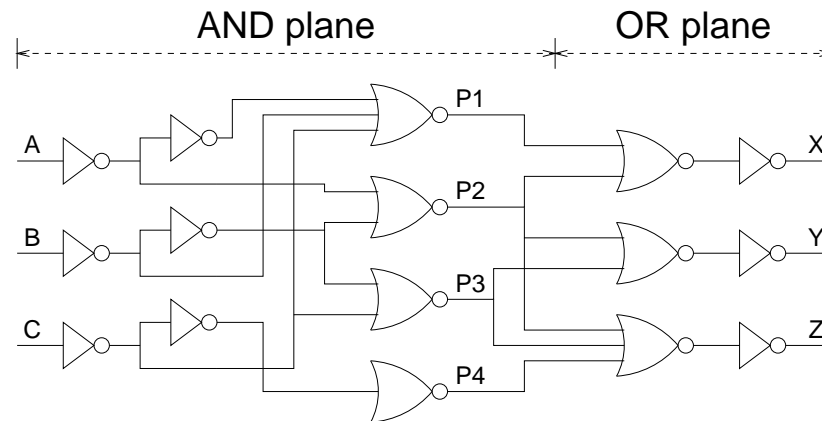


# PLAs, ROMs and RAMs

---
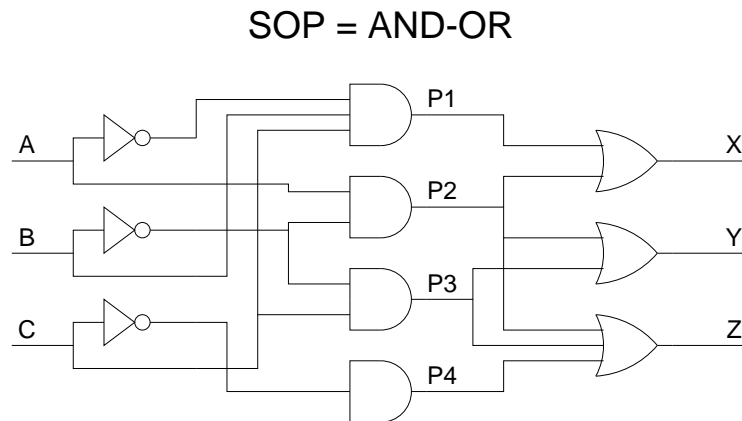
## PLA structures

Programmable Logic Array structures provide a logical and compact method of implementing multiple SOP (Sum of Products) or POS expressions.




Most PLA structures employ pseudo-NMOS NOR gates using a P-channel device in place of the NMOS depletion load.

# PLAs, ROMs and RAMs

---


## Pseudo-NMOS NOR gate

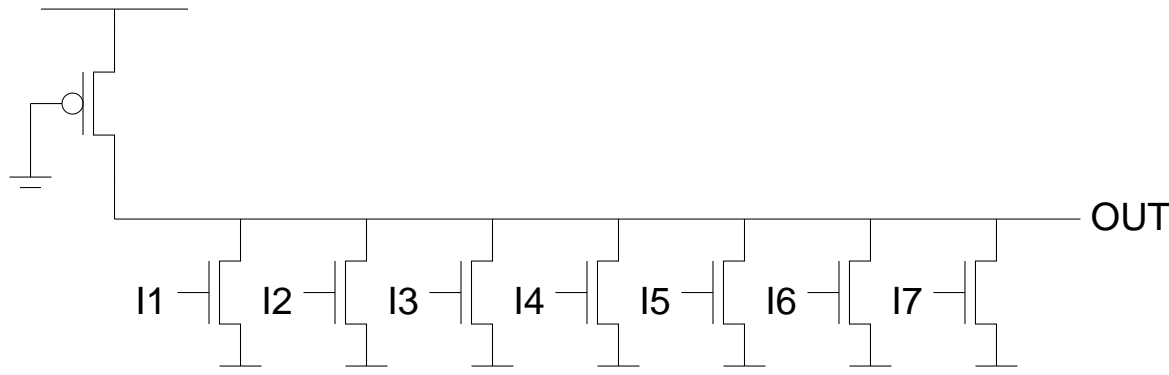

- Unlike complementary CMOS circuits, these gates will dissipate power under static conditions (since the P device is always on).
- The P and N channel devices must be ratioed in order to create the required low output voltage.
- This ratioing results in a slower gate, although there is a trade-off between gate speed and static power dissipation.

# PLAs, ROMs and RAMs

## PLA structure

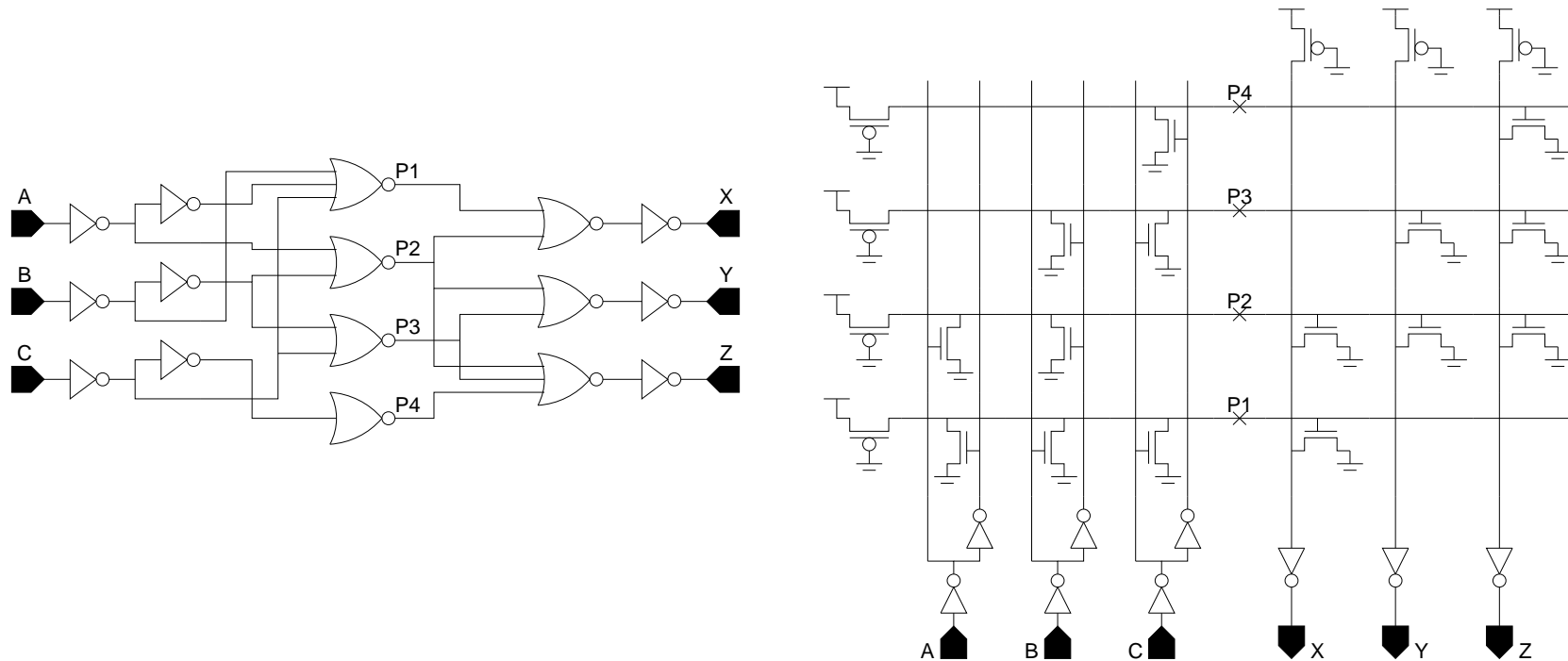


- A regular layout is employed, with columns for inputs and outputs and rows for intermediate expressions.

# PLAs, ROMs and RAMs

---


## PLA structure

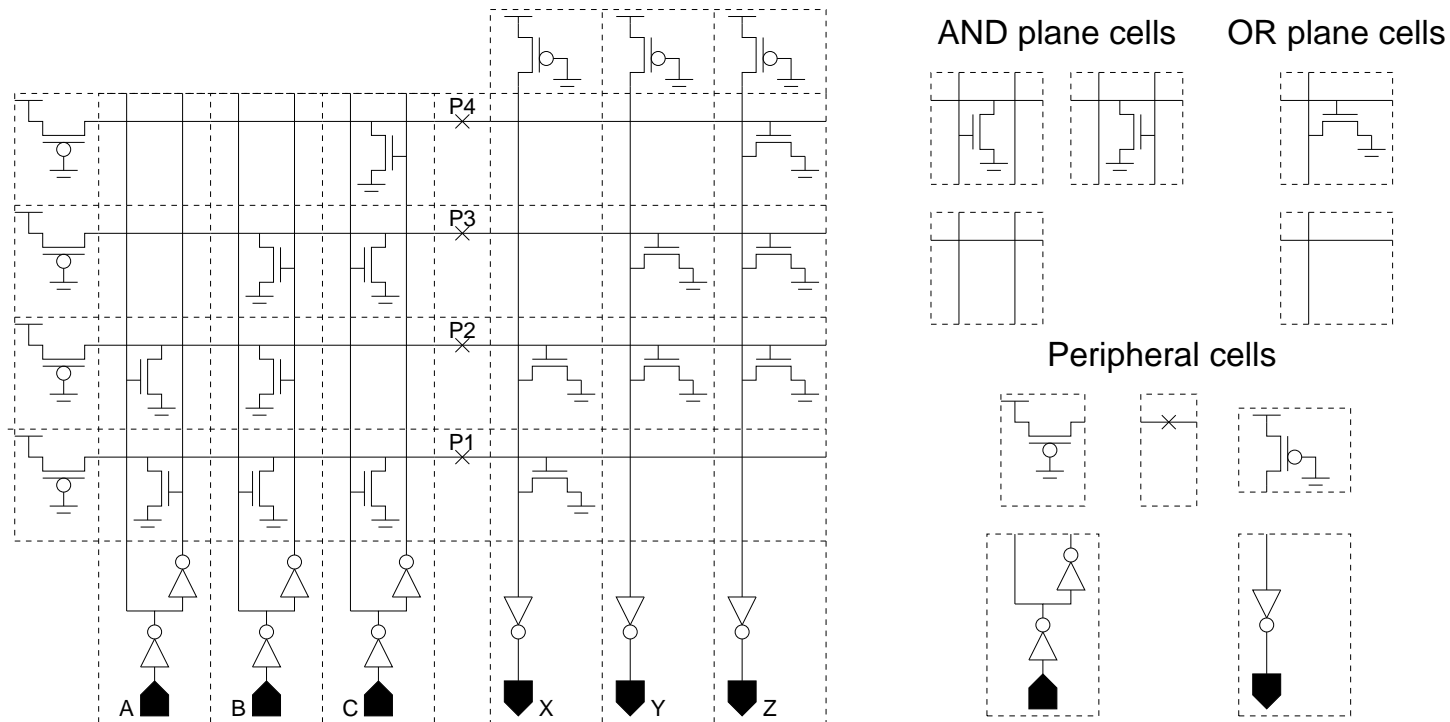

- Layout is simply a matter of selecting and placing rectangular cells from a limited set.

# PLAs, ROMs and RAMs

## PLA structure

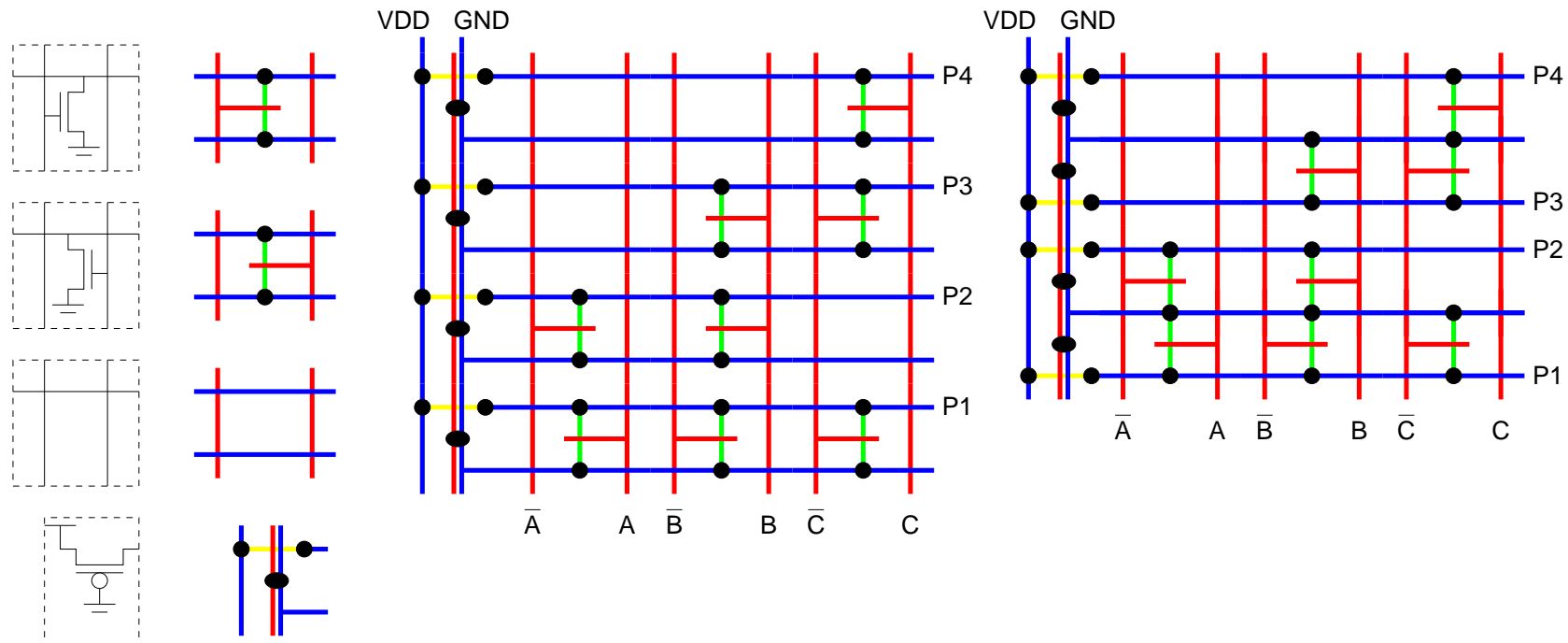


- Conversion to *sticks* is straight forward with opportunities for further optimization.

# PLAs, ROMs and RAMs

---
 
## ROMs

- A ROM may simply be a PLA with fixed decoder plane<sup>1</sup> and programmable data plane.



---


<sup>1</sup>RAM structures can make use of the same decode plane.

# PLAs, ROMs and RAMs

---
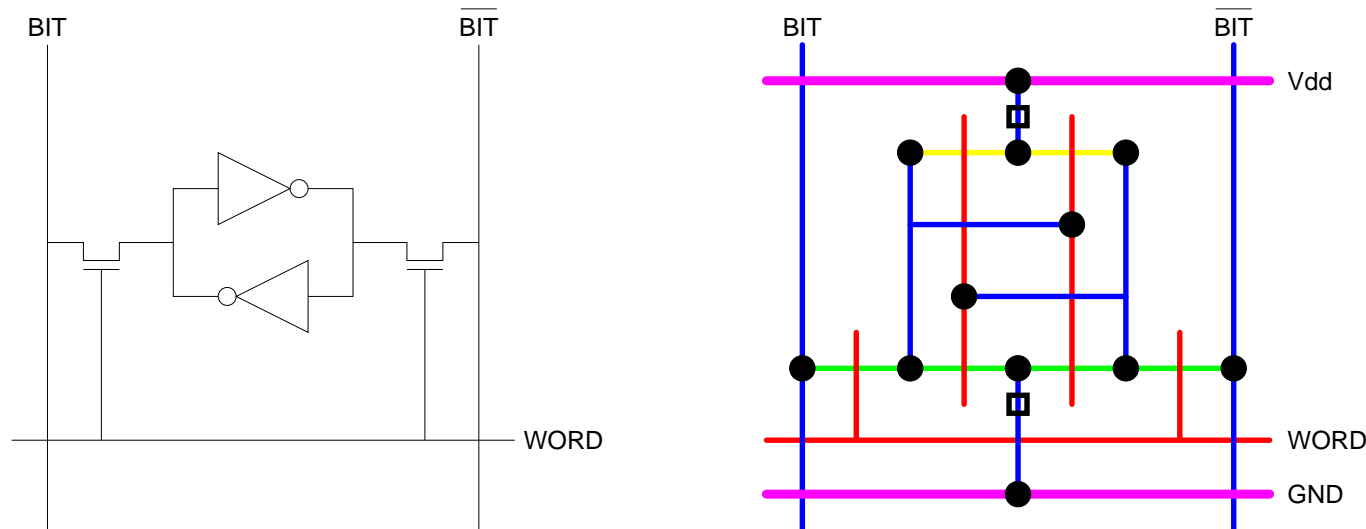
## Static RAM

- Used for high density storage on a standard CMOS process.
- Short lived conflict during write - NMOS transistors offer stronger path.
- Differential amplifiers are used for speedy read.



Standard 6 transistor static RAM cell.

